

# Lab 7

## 16-bit Barrel Shifter / Rotator & 4-Digit 7-Segment Display

By: Ben Robles & Robert Stevenson  
Group U

ECE-3300L  
Summer 2026

Date: 07/30/2026

# Design:

## clock\_divider\_fixed.v:

```
module clock_divider_fixed(
    input wire clk_100MHz,
    output reg clk_2Hz,
    output reg clk_1kHz
);

reg [15:0] counter_1kHz;
reg [7:0] counter_2Hz;

initial begin
    counter_2Hz = 0;
    counter_1kHz = 0;
    clk_2Hz = 0;
    clk_1kHz = 0;
end

always @(posedge clk_100MHz) begin
    if(counter_1kHz == 16'd49_999) begin // 100MHz / (2 x 50000) = 1kHz
        counter_1kHz <= 0;
        clk_1kHz <= ~clk_1kHz;
    end
    else counter_1kHz <= counter_1kHz + 1'b1;
end

always @(posedge clk_1kHz) begin
    if(counter_2Hz == 8'd249) begin // 1kHz / (2 * 250) = 2Hz
        counter_2Hz <= 0;
        clk_2Hz <= ~clk_2Hz;
    end
    else counter_2Hz <= counter_2Hz + 1'b1;
end

endmodule
```

## Description:

This module takes a 100MHz clock and outputs a 1kHz and 2 Hz clock. This is done by a counter and the formula  $f_{out} = f_{in} / 2 * \text{counter}$ . The first counter to create the 1 kHz clock increments to 50k ( $100\text{MHz} / (2 \times 50000) = 1\text{kHz}$ ) while the 2 Hz clock cascades off the 1 kHz clock at 4 times the frequency ( $1\text{kHz} / (2 * 250) = 2\text{Hz}$ )

## debounce\_toggle.v:

```
module debounce_toggle(
    input wire btn_raw,
    input wire clk_1kHz,
    input wire rst_n,
```

```

        output reg btn_toggle
    );
    // Debounce
    reg [2:0] btn_val;
    reg btn_clean;
    reg btn_prev;

    always @(posedge clk_1kHz or negedge rst_n) begin
        if(!rst_n) begin
            btn_val = 3'b000;
            btn_clean = 1'b0;
        end
        else begin
            btn_val = {btn_val[1:0], btn_raw};
            if(btn_val == 3'b111) btn_clean = 1;
            else if(btn_val == 3'b000) btn_clean = 0;
        end
    end

    // Toggle
    always @(posedge clk_1kHz or negedge rst_n) begin
        if (!rst_n) begin
            btn_toggle <= 1'b0;
            btn_prev <= 1'b0;
        end
        else begin
            if(btn_clean && !btn_prev)
                btn_toggle <= ~btn_toggle;

            btn_prev <= btn_clean;
        end
    end
endmodule

```

## Description:

This module combines the debounce module and toggle module from previous labs. Debounce is achieved by verifying a steady 3-bit input and toggle acts as a latch.

## barrel\_shifter16.v:

```

module barrel_shifter16(
    input [15:0] data_in,
    input [3:0] shamt,
    input dir,
    input rotate,
    output wire [15:0] data_out
);

    reg [15:0] stage1_in;
    reg [15:0] stage2_in;
    reg [15:0] stage3_in;
    reg [15:0] stage4_in;

```

```

wire [15:0] stage0;
wire [15:0] stage1_out;
wire [15:0] stage2_out;
wire [15:0] stage3_out;
wire [15:0] stage4_out;

genvar i;

assign stage0 = data_in;

always @(*)
begin
    case ({rotate, dir})
        2'b00: begin // Shift left
            stage1_in = {stage0[14:0], 1'b0};
            stage2_in = {stage1_out[13:0], 2'b00};
            stage3_in = {stage2_out[11:0], 4'b0000};
            stage4_in = {stage3_out[7:0], 8'b00000000};
        end
        2'b01: begin // Shift right
            stage1_in = {1'b0, stage0[15:1]};
            stage2_in = {2'b00, stage1_out[15:2]};
            stage3_in = {4'b0000, stage2_out[15:4]};
            stage4_in = {8'b00000000, stage3_out[15:8]};
        end
        2'b10: begin // Rotate left
            stage1_in = {stage0[14:0], stage0[15]};
            stage2_in = {stage1_out[13:0], stage1_out[15:14]};
            stage3_in = {stage2_out[11:0], stage2_out[15:12]};
            stage4_in = {stage3_out[7:0], stage3_out[15:8]};
        end
        2'b11: begin // Rotate right
            stage1_in = {stage0[0], stage0[15:1]};
            stage2_in = {stage1_out[1:0], stage1_out[15:2]};
            stage3_in = {stage2_out[3:0], stage2_out[15:4]};
            stage4_in = {stage3_out[7:0], stage3_out[15:8]};
        end
    endcase
end

generate
    for (i = 0; i < 16; i = i + 1) begin
        mux2x1 mux_stage1(
            .a(stage0[i]),
            .b(stage1_in[i]),
            .sel(shamt[0]),
            .y(stage1_out[i])
        );
    end

    for (i = 0; i < 16; i = i + 1) begin
        mux2x1 mux_stage2(
            .a(stage1_out[i]),
            .b(stage2_in[i]),
            .sel(shamt[1]),
            .y(stage2_out[i])
        );
    end

    for (i = 0; i < 16; i = i + 1) begin

```

```

        mux2x1 mux_stage3(
            .a(stage2_out[i]),
            .b(stage3_in[i]),
            .sel(shamt[2]),
            .y(stage3_out[i])
        );
    end

    for (i = 0; i < 16; i = i + 1) begin
        mux2x1 mux_stage4(
            .a(stage3_out[i]),
            .b(stage4_in[i]),
            .sel(shamt[3]),
            .y(stage4_out[i])
        );
    end
endgenerate

assign data_out = stage4_out;

endmodule

```

## Description:

This module uses a log-stage barrel shifter to operate on a 16-bit input. At 4 stages and 16 muxes per stage, this design uses 64 total muxes generated by LUTS. The operation is selected by inputs to change direction and rotation, while the input "shamt" determines what stages of the shifter the input will go through

## shamt\_counter.v:

```

module shamt_counter(
    input wire clk_1kHz,
    input wire btn_raw,
    output reg [1:0] shamt_high
);

    reg [2:0] btn_val;
    reg btn_clean;
    reg btn_prev;

    initial begin
        btn_val = 3'b000;
        btn_clean = 1'b0;
        btn_prev = 1'b0;
        shamt_high = 2'b00;
    end

    always @(posedge clk_1kHz) begin
        btn_prev = btn_clean;
        btn_val = {btn_val[1:0], btn_raw};

        if(btn_val == 3'b111) btn_clean = 1;
        else if(btn_val == 3'b000) btn_clean = 0;
    end
endmodule

```

```

        if(btn_clean && !btn_prev)
            shamt_high = shamt_high + 1'b1;
        end

endmodule

```

## Description:

Shamt counter uses a 2-bit free counter that advances on a button press. In order to circumvent the dual purpose asynchronous reset the button is also used for, this module replicates the debounce module internally

## hex\_to\_7seg.v:

```

module hex_to_7seg(
    input [3:0] hex,
    output reg [6:0] digit
);

always @(*) begin
    case(hex)
        4'd0: digit=7'b0000001;
        4'd1: digit=7'b1001111;
        4'd2: digit=7'b0010010;
        4'd3: digit=7'b0000110;
        4'd4: digit=7'b1001100;
        4'd5: digit=7'b0100100;
        4'd6: digit=7'b0100000;
        4'd7: digit=7'b0001111;
        4'd8: digit=7'b0000000;
        4'd9: digit=7'b0001100;
        4'd10: digit=7'b0001000;
        4'd11: digit=7'b1100000;
        4'd12: digit=7'b0110001;
        4'd13: digit=7'b1000010;
        4'd14: digit=7'b0110000;
        4'd15: digit=7'b0111000;
        default: digit=7'b1111111;
    endcase
end

endmodule

```

## Description:

This module is a simple hex lookup table for the active low 7seg display

## seg7\_scan8.v:

```

module seg7_scan8(

```

```

        input clk_1kHz,
        input rst_n,
        input [15:0] word,
        output reg [7:0] an,
        output reg [6:0] seg
    );

    reg [2:0] sel;

    wire [6:0] digit0;
    wire [6:0] digit1;
    wire [6:0] digit2;
    wire [6:0] digit3;

    hex_to_7seg hex0(
        .hex(word[3:0]),
        .digit(digit0)
    );

    hex_to_7seg hex1(
        .hex(word[7:4]),
        .digit(digit1)
    );

    hex_to_7seg hex2(
        .hex(word[11:8]),
        .digit(digit2)
    );

    hex_to_7seg hex3(
        .hex(word[15:12]),
        .digit(digit3)
    );

    always @(posedge clk_1kHz or negedge rst_n) begin
        if(!rst_n)
            sel <= 3'b000;
        else
            sel <= sel + 1'b1;
    end

    always @(*) begin
        case(sel)
            3'd0: begin
                an = 8'b11111110;
                seg = digit0;
            end
            3'd1: begin
                an = 8'b11111101;
                seg = digit1;
            end
            3'd2: begin
                an = 8'b11111011;
                seg = digit2;
            end
            3'd3: begin
                an = 8'b11110111;
                seg = digit3;
            end
            default: begin
                an = 8'b11111111;

```

```

        seg = 7'b1111111;
    end
endcase
end

endmodule

```

## Description:

This scanner uses the hex\_to\_7seg module four times in order to determine each digit it will display to the 7seg. On each 1 kHz clock cycle a different display is driven with its corresponding digit, including the unused upper displays that are turned off.

## top\_lab7.v:

```

module top_lab7(
    input CLK_100MHz,
    input [15:0] SW,
    input BTNC, BTNU, BTND, BTNL, BTNR,
    output wire [7:0] AN,
    output wire [6:0] SEG,
    output wire [7:0] LED
);

wire RST_N;
assign RST_N = ~BTNC;

wire CLK_1kHz;
wire CLK_2Hz;

wire DIR;
wire ROTATE;

wire [1:0] SHAMT_LOW;
wire [1:0] SHAMT_HIGH;

wire [15:0] BARREL_OUT;
wire [15:0] RESULT_WORD;

clock_divider_fixed clk_divs(
    .clk_100MHz(CLK_100MHz),
    .clk_2Hz(CLK_2Hz),
    .clk_1kHz(CLK_1kHz)
);

debounce_toggle debounce_btnu(
    .btn_raw(BTNU),
    .clk_1kHz(CLK_1kHz),
    .rst_n(RST_N),
    .btn_toggle(DIR)
);

debounce_toggle debounce_btnd(
    .btn_raw(BTND),

```



```

        .clk_1kHz(CLK_1kHz),
        .rst_n(RST_N),
        .btn_toggle(ROTATE)
    );

    debounce_toggle debounce_btnl(
        . btn_raw(BTNL),
        .clk_1kHz(CLK_1kHz),
        .rst_n(RST_N),
        .btn_toggle(SHAMT_LOW[1])
    );

    debounce_toggle debounce_btnr(
        . btn_raw(BTNR),
        .clk_1kHz(CLK_1kHz),
        .rst_n(RST_N),
        .btn_toggle(SHAMT_LOW[0])
    );

    shamt_counter shamt_count(
        .clk_1kHz(CLK_1kHz),
        .btn_raw(BTNC),
        .shamt_high(SHAMT_HIGH)
    );

    barrel_shifter16 shifter(
        .data_in(SW),
        .shamt({SHAMT_HIGH, SHAMT_LOW}),
        .dir(DIR),
        .rotate(ROTATE),
        .data_out(BARREL_OUT)
    );

    assign RESULT_WORD = BARREL_OUT;

    seg7_scan8 display(
        .clk_1kHz(CLK_1kHz),
        .rst_n(RST_N),
        .word(RESULT_WORD),
        .an(AN),
        .seg(SEG)
    );

    assign LED = {DIR, ROTATE, 2'b00, {SHAMT_HIGH, SHAMT_LOW}};

endmodule

```

## Description:

The top level module instantiates and wires each module together as well as displaying LED readouts.

# XDC Snippet:

```
# Clock signal
set_property -dict { PACKAGE_PIN E3   IOSTANDARD LVCMOS33 } [get_ports { CLK_100MHz }]; #IO_L12P_T1_MRCC_35
Sch=clk100mhz
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {CLK_100MHz}];
```

## ##Switches

```
set_property -dict { PACKAGE_PIN J15   IOSTANDARD LVCMOS33 } [get_ports { SW[0] }];
set_property -dict { PACKAGE_PIN L16   IOSTANDARD LVCMOS33 } [get_ports { SW[1] }];
set_property -dict { PACKAGE_PIN M13   IOSTANDARD LVCMOS33 } [get_ports { SW[2] }];
...
set_property -dict { PACKAGE_PIN U12   IOSTANDARD LVCMOS33 } [get_ports { SW[13] }];
set_property -dict { PACKAGE_PIN U11   IOSTANDARD LVCMOS33 } [get_ports { SW[14] }];
set_property -dict { PACKAGE_PIN V10   IOSTANDARD LVCMOS33 } [get_ports { SW[15] }];
```

## ## LEDs

```
set_property -dict { PACKAGE_PIN H17   IOSTANDARD LVCMOS33 } [get_ports { LED[0] }];
set_property -dict { PACKAGE_PIN K15   IOSTANDARD LVCMOS33 } [get_ports { LED[1] }];
...
set_property -dict { PACKAGE_PIN U17   IOSTANDARD LVCMOS33 } [get_ports { LED[6] }];
set_property -dict { PACKAGE_PIN U16   IOSTANDARD LVCMOS33 } [get_ports { LED[7] }];
```

## #7 segment display

```
set_property -dict { PACKAGE_PIN T10   IOSTANDARD LVCMOS33 } [get_ports { SEG[6] }];
set_property -dict { PACKAGE_PIN R10   IOSTANDARD LVCMOS33 } [get_ports { SEG[5] }];
...
set_property -dict { PACKAGE_PIN T11   IOSTANDARD LVCMOS33 } [get_ports { SEG[1] }];
set_property -dict { PACKAGE_PIN L18   IOSTANDARD LVCMOS33 } [get_ports { SEG[0] }];

set_property -dict { PACKAGE_PIN J17   IOSTANDARD LVCMOS33 } [get_ports { AN[0] }];
set_property -dict { PACKAGE_PIN J18   IOSTANDARD LVCMOS33 } [get_ports { AN[1] }];
set_property -dict { PACKAGE_PIN T9    IOSTANDARD LVCMOS33 } [get_ports { AN[2] }];
...
set_property -dict { PACKAGE_PIN T14   IOSTANDARD LVCMOS33 } [get_ports { AN[5] }];
set_property -dict { PACKAGE_PIN K2    IOSTANDARD LVCMOS33 } [get_ports { AN[6] }];
set_property -dict { PACKAGE_PIN U13   IOSTANDARD LVCMOS33 } [get_ports { AN[7] }];
```

## #Buttons

```
set_property -dict { PACKAGE_PIN N17   IOSTANDARD LVCMOS33 } [get_ports { BTNC }]; #IO_L9P_T1_DQS_14 Sch=btnc
set_property -dict { PACKAGE_PIN M18   IOSTANDARD LVCMOS33 } [get_ports { BTNU }]; #IO_L4N_T0_D05_14 Sch=btneu
set_property -dict { PACKAGE_PIN P17   IOSTANDARD LVCMOS33 } [get_ports { BTNL }]; #IO_L12P_T1_MRCC_14 Sch=btntl
set_property -dict { PACKAGE_PIN M17   IOSTANDARD LVCMOS33 } [get_ports { BTNR }]; #IO_L10N_T1_D15_14 Sch=btnr
set_property -dict { PACKAGE_PIN P18   IOSTANDARD LVCMOS33 } [get_ports { BTND }]; #IO_L9N_T1_DQS_D13_14 Sch=btnd
```

# Simulation:

## seg7\_scan8\_TB.v:

```
module seg7_scan8_TB(

    );

    reg clk_tb;
    reg rst_n_tb;

    reg [15:0] word_tb;

    wire [7:0] an_tb;
    wire [6:0] seg_tb;

    reg [7:0] expected_an;
    reg [6:0] expected_seg;

    integer i;
    integer tasksfailed;

    seg7_scan8 scan_tb(
        .clk_1kHz(clk_tb),
        .rst_n(rst_n_tb),
        .word(word_tb),
        .an(an_tb),
        .seg(seg_tb)
    );

    initial
    begin
        clk_tb = 1'b0;
        rst_n_tb = 1'b0;

        word_tb = 16'hDCBA;

        tasksfailed = 0;
    end

    always
    begin
        #5 clk_tb = ~clk_tb;
    end

    initial
    begin
        @(posedge clk_tb);
        #1;
        rst_n_tb = 1'b1;

        for(i = 0; i < 8; i = i + 1) begin
            case(i)
                0: begin
                    expected_an = 8'b11111110;
                    expected_seg = 7'b0001000;
                end
            end
        end
    end
endmodule
```

```

1: begin
    expected_an = 8'b11111101;
    expected_seg = 7'b1100000;
end

2: begin
    expected_an = 8'b11111011;
    expected_seg = 7'b0110001;
end

3: begin
    expected_an = 8'b11110111;
    expected_seg = 7'b1000010;
end

default: begin
    expected_an = 8'b11111111;
    expected_seg = 7'b1111111;
end
endcase

if((an_tb !== expected_an) || (seg_tb !== expected_seg))
begin
    tasksfailed = tasksfailed + 1;
    $display("FAILED: Digit = %d:  AN = %b, expected = %b  SEG = %b, expected = %b", i, an_tb, expected_an, seg_tb,
expected_seg);
end

if(i < 7) begin
    @(posedge clk_tb)
    #1;
end
end

if(tasksfailed == 0)
    $display("All tests passed");
else
    $display("%d tests failed", tasksfailed);

$finish;
end
endmodule

```

## Description:

To check 1-of-8 enable sequence and segment codes, I input a distinct word "DCBA" and used automatic checks to verify the correct digit and display was active each clock cycle.


## Output:

```

All tests passed
$finish called at time : 76 ns : File "D:/School/ECE3300/ECE3300 Lab7 GroupU

```

## Waveform:

 

## debounce\_toggle\_TB.v:

```
module debounce_toggle_TB(

    );

    reg clk_tb;
    reg btn_raw_tb;
    reg rst_n_tb;
    wire btn_toggle_tb;

    debounce_toggle db_tb(
        .clk_1kHz(clk_tb),
        .btn_raw(btn_raw_tb),
        .rst_n(rst_n_tb),
        .btn_toggle(btn_toggle_tb)
    );

    initial
    begin
        clk_tb = 1'b0;
        rst_n_tb = 1'b0;
    end

    always
    begin
        #5 clk_tb = ~clk_tb;
    end

    initial
    begin
        @(posedge clk_tb)
        #1;
        rst_n_tb = 1'b1;

        btn_raw_tb = 1'b0;          // Test 1: Stable low
        repeat(6) @(posedge clk_tb);
        #1;

        if(btn_toggle_tb !== 1'b0)
        begin
            $display("FAIL: btn_toggle should be 0 after stable low");
            $fatal;
        end
    end
```

```

    btn_raw_tb = 1'b1;          // Test 2: Bounce
    @(posedge clk_tb);
    #1;

    btn_raw_tb = 1'b0;
    @(posedge clk_tb);
    #1;

    if(btn_toggle_tb !== 1'b0)
    begin
        $display("FAIL: btn_toggle changed after bounce");
        $fatal;
    end

    btn_raw_tb = 1'b1;          // Test 3: Toggle on
    repeat(6) @(posedge clk_tb);
    #1;
    btn_raw_tb = 1'b0;
    repeat(6) @(posedge clk_tb);

    if(btn_toggle_tb !== 1'b1)
    begin
        $display("FAIL: btn_toggle should be 1 after stable high");
        $fatal;
    end

    btn_raw_tb = 1'b1;          // Test 4: Bounce
    @(posedge clk_tb);
    #1;

    btn_raw_tb = 1'b0;
    @(posedge clk_tb);
    #1;

    if(btn_toggle_tb !== 1'b1)
    begin
        $display("FAIL: btn_toggle changed after bounce");
        $fatal;
    end

    btn_raw_tb = 1'b1;          // Test 3: Toggle off
    repeat(6) @(posedge clk_tb);
    #1;
    btn_raw_tb = 1'b0;
    repeat(6) @(posedge clk_tb);

    if(btn_toggle_tb !== 1'b0)
    begin
        $display("FAIL: btn_toggle should be 0 after stable high");
        $fatal;
    end

    $display("Passed all tests");
    $finish;
end

endmodule

```

## Description:


To verify the debounce and toggle implementation we tested random bounces and automatically verified that they were filtered. We also tested that toggle only switches on active high

## Output:

```
Passed all tests
```

```
$finish called at time : 345 ns : File "D:/School/ECE3300/ECE3300 Lab7 GroupU/ECE3300 Lab7 GroupU
```

## Waveform:

 

## barrel\_shifter16\_TB.v:

```
module barrel_shifter16_TB( );

    wire [15:0] result;
    reg [15:0] check_val;
    reg [15:0] in_val;
    reg [3:0] shamt;
    reg dir, rot;

    barrel_shifter16 barrel_TB(.data_in(in_val),
    .shamt(shamt), .dir(dir), .rotate(rot), .data_out(result));

    integer i, j, tasksfailed;
    initial begin
        in_val = 16'b0;
        shamt = 4'b0;
        check_val = 0;
        i = 0;
        tasksfailed = 0;
        //Rotate Right
        dir = 1;
        rot = 1;
        in_val = 16'hFAC3;
        check_val = {in_val[14:0], in_val[15]};
        for(j = 0; j < 16; j = j + 1)begin
            shamt = j;
            check_val = {check_val[0], check_val[15:1]};
            #10;
            if(result != check_val)begin
                tasksfailed = tasksfailed + 1;
            end
        end
    end
endmodule
```

```

        $display("Test Failed at %d", j);
    end
end

//Rotate Left
dir = 0;
rot = 1;
in_val = 16'hFAC3;
check_val = {in_val[0], in_val[15:1]};
for(j = 0; j < 16; j = j + 1)begin
    shamt = j;
    check_val = {check_val[14:0], check_val[15]};
    #10;
    if(result != check_val)begin
        tasksfailed = tasksfailed + 1;
        $display("Test Failed at %d", j);
    end
end

//Logical Shift Right
dir = 1;
rot = 0;
in_val = 16'h8000;
check_val = 16'h0001;
for(j = 0; j < 16; j = j + 1)begin
    shamt = j;
    check_val = {check_val[0], check_val[15:1]};
    #10;
    if(result != check_val)begin
        tasksfailed = tasksfailed + 1;
        $display("Test Failed at %d", j);
    end
end

//Logical Shift Left
dir = 0;
rot = 0;
in_val = 16'b1;
check_val = 16'h8000;
for(j = 0; j < 16; j = j + 1)begin
    shamt = j;
    check_val = {check_val[14:0], check_val[15]};
    #10;
    if(result != check_val)begin
        tasksfailed = tasksfailed + 1;
        $display("Test Failed at %d", j);
    end
end
$display("%d Tests failed", tasksfailed);
$finish;
end

endmodule

```




## Description:

In this test bench the barrel shifter module is tested with an input, FAC3, which generates unique outputs for any size of shift in the rotate setting. This input is shifted through all sixteen bits in both directions. To test the logical shift a single bit is set and shifted through all sixteen bit positions, demonstrating the functionality of the barrel shifter.

## Output:

```
Time resolution is 1 ps
0 Tests failed
$finish called at time : 640 ns : File "C:/Users/rbSte/Documents/ECE_3300/ECE_3300_Lab/ECE_3300_Lab/ECE3300-Lab7-GroupU/Simulation/barrel
```

## Waveform:

 



# Implementation:

## Resource Utilization Report:

| Name                | <sup>1</sup> | Slice LUTs<br>(63400) | Slice Registers<br>(126800) | F7 Muxes<br>(31700) | Slice<br>(15850) | LUT as Logic<br>(63400) | Bonded IOB<br>(210) | BUFGCTRL<br>(32) |
|---------------------|--------------|-----------------------|-----------------------------|---------------------|------------------|-------------------------|---------------------|------------------|
| > <b>N</b> top_lab7 |              | 113                   | 45                          | 7                   | 44               | 113                     | 45                  | 1                |

## Timing Report:

### Design Timing Summary

| Setup                                | Hold                             | Pulse Width                                       |
|--------------------------------------|----------------------------------|---------------------------------------------------|
| Worst Negative Slack (WNS): 5.865 ns | Worst Hold Slack (WHS): 0.265 ns | Worst Pulse Width Slack (WPWS): 4.500 ns          |
| Total Negative Slack (TNS): 0.000 ns | Total Hold Slack (THS): 0.000 ns | Total Pulse Width Negative Slack (TPWS): 0.000 ns |
| Number of Failing Endpoints: 0       | Number of Failing Endpoints: 0   | Number of Failing Endpoints: 0                    |
| Total Number of Endpoints: 33        | Total Number of Endpoints: 33    | Total Number of Endpoints: 18                     |

All user specified timing constraints are met.

## Group Video:

<https://youtu.be/esJ6hO58ZkA>

## Contributions:

Robert Stevenson: Core design, testbenches

Ben Robles: Design/Implementation, testbenches

## Reflections:

Ben Robles: I enjoyed tackling more complex combinational logic and RTL design in this lab as well as continuing to build off the modules we've been working on. This lab was harder than the last, but not too bad at all.

Robert Stevenson: I enjoyed this lab, it was interesting and enjoyable to work on these complex combinational circuits. Although little of my original design for the barrel shifter made it to the final design, it was an enjoyable experience to overcome the challenge of designing a functional, if inelegant, barrel shifter.